

Lecture 2: Piffles in  $\mathbb{Z}^d$ 

Week 5

Mathcamp 2011

Yesterday, we showed that electrical networks and random walks are remarkably related subjects. Today, I want to use these connections to study a question of Polya:

**Question 1** *Suppose you've lost a piffle (i.e. a random walker) at some point in the integer lattice  $\mathbb{Z}^d$ ! Suppose your home is at the origin. Given enough time, will the piffle return home?*

## 1 Circuits as Black Boxes

To attack this kind of question, it might help to introduce some new ideas. Specifically, suppose that we have a circuit with two points  $a, b$ , where we've grounded  $a$  and have a voltage  $v$  established at  $b$ . Then there is some amount of current flowing out of  $b$ : this current  $i_b$  is the sum of the currents  $\sum_{x \in N(b)} i_{bx}$ .

Mentally, we can think of this entire circuit as just a large and bulky resistor – we have applied a voltage across two points, and a current is flowing across the circuit. Specifically, if we think of this object as a large resistor, we know that its resistance can be found by applying Ohm's law: call this quantity  $R_{\text{eff}}$ , and set it equal to  $v(b)/i_b$ . Similarly, define  $C_{\text{eff}} = 1/R_{\text{eff}}$ .

Earlier, we noted that the current across an edge  $(x, y)$  was proportional to the expected number of paths from  $x$  to  $y$  minus the expected number of paths from  $y$  to  $x$ , if the voltage we put out of  $b$  was equal to 1 (say.) Does this idea still hold here? Well: calculating, we have


$$\begin{aligned}
 i_b &= \sum_{x \in N(b)} (v(b) - v(y)) \cdot C_{by} \\
 &= \sum_{x \in N(b)} (v(b) - v(y)) \cdot \frac{C_{by}}{C_b} \cdot C_b \\
 &= C_b \left( v(b) \sum_{x \in N(b)} \frac{C_{by}}{C_b} - \sum_{x \in N(b)} \frac{C_{by}v(y)}{C_b} \right) \\
 &= C_b \left( 1 - \sum_{x \in N(b)} v(y) \frac{C_{by}}{C_b} \right) \\
 &= C_b \left( 1 - \sum_{x \in N(b)} v(y) P_{by} \right).
 \end{aligned}$$

What is this last quantity? Well:  $P_{by}$  denotes the probability of going from  $b$  to  $y$ , and (as we saw yesterday)  $v(y)$  is the probability that a walk starting at  $y$  will make it to  $b$  before  $a$ . So: if we're starting at  $b$  and leaving to any of  $b$ 's neighbors (which we pick with probability  $P_{by}$ ), the chances of returning to  $b$  before making it to  $a$  is just  $v(y)$ . Therefore, the sum on the inside of our parentheses is precisely the chances of starting at  $b$  and returning there before making it to  $a$ : therefore, the entire quantity is just  $C_b$  multiplied by the chances of a walk starting at  $b$  and making it to  $a$  before returning to  $b$ . Call the chance of this occurring  $p_{\text{esc}}$ : then, we have just shown that

$$\frac{i_b}{C_b} = p_{\text{esc}}.$$
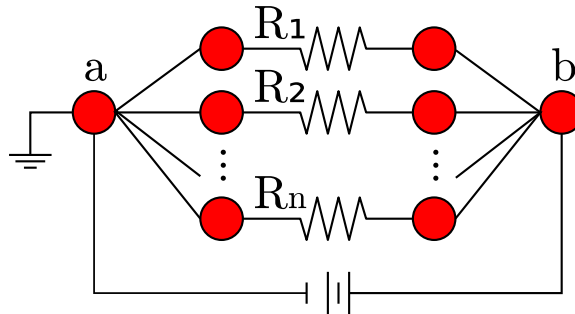
## 2 Resistance: Surprisingly Not Futile

This, basically, is **win**. Specifically: we know how to find resistances! Super-specifically: suppose we have a series of resistors connected “in parallel,” i.e. like in the picture below:




Then the effective resistance of the pictured circuit is the reciprocal of the sum of the reciprocals of the resistors:

$$\frac{1}{R_{\text{eff}}} = \sum_{i=1}^n \frac{1}{R_i}.$$

Alternately, you can think of this claim as the statement that the “effective conductance” of the circuit is the sum of the conductances of the circuit.

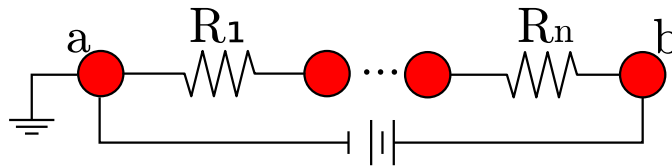Similarly, suppose we have a circuit made of resistors linked in series, as depicted below:



Then the effective resistance of the pictured circuit is the sum of the resistors:

$$R_{\text{eff}} = \sum_{i=1}^n R_i.$$

It bears noting that you can deduce these properties from the two rules we've stated for electrical networks, Ohm's law and Kirchoff's law; the first property just says that the conductances sum when we have resistors in parallel, and the second says that resistances sum when we have resistors in series. We omit a formal proof here, but it's not remotely difficult.

The other property of electrical networks we're going to use throughout our proofs is Rayleigh's Monotonicity Theorem, which we state here:

**Theorem 2** *If any of the individual resistances in a circuit increase, then the overall effective resistance of the circuit can only increase or stay constant; conversely, if any of the individual resistances in a circuit decrease, the overall effective resistance of the circuit can only decrease or stay constant.*

*In specific, cutting wires (setting certain resistances to infinity) only increases the effective resistance, while fusing vertices together (setting certain resistances to 0) only decreases the effective resistance.*

We also omit the proof of the statement here; it's actually somewhat involved, but can be proven directly from our two laws without any appeal to electrical networks in "reality."

### 3 Piffles in $\mathbb{Z}^d$

Given these tools, we are now equipped to tackle our question! Let's turn to  $\mathbb{Z}^1$ , as a quick warm-up. Our question, then, is whether a piffle starting at some point on the lattice (say the origin) will always return to the origin, or whether there's a nonzero chance that it wanders off forever.

We only have the tools to talk about finite graphs. To turn these tools into ones to deal with an infinite connected graph  $G$ , do the following:

- Let  $x$  be whichever node we're designating as the origin, and  $G^{(r)}$  be the graph formed by taking all of the vertices connected to  $x$  by paths of length at most  $r$ .
- Turn this into an electrical network problem by soldering all of the vertices that are distance  $r$  from  $x$  together into one big ball, grounding them, and putting one unit of voltage at  $x$ , and making all of the edges resistors with resistance 1. Then, via our earlier discussions, we can talk about the probability that a piffle starting at  $x$  will make it to distance  $r$  before returning to  $x$ : denote this quantity as  $p_{\text{esc}}^{(r)}$ .
- Let  $p_{\text{esc}}$  be the limit  $\lim_{r \rightarrow \infty} p_{\text{esc}}^{(r)}$ . If this is nonzero, then there is some nonzero chance that our piffle will wander forever; if this is zero, then our piffle must eventually return to the origin.
- Notice that if it must eventually return to the origin, then it must eventually make it to any vertex  $w$  in  $G$ ! This is because starting from the origin, we always have some nonzero chance to make it to  $w$ , and (because we return to the origin infinitely many times) we get infinitely many tries.

If  $G$  is a graph on which we return infinitely many times to the origin, we call  $G$  **recurrent**; if it is a graph where there is a chance that we will never return to the origin, we call  $G$  **transient**.

**Theorem 3** *The one-dimensional lattice graph  $\mathbb{Z}$  is recurrent.*

**Proof.** Let 0 be the origin, without any loss of generality. Using our earlier discussion, we know that

$$p_{\text{esc}}^{(r)} = \frac{i_0}{C_0} = \frac{1}{C_0} \cdot \frac{v(0)}{R_{\text{eff}}} = \frac{1}{C_0 R_{\text{eff}}}.$$

We know that the resistance of a string of  $r$  resistors in a row is  $r$ , from our earlier discussion about resistors in series: as there are two such strings in parallel, we know that their combined resistance is  $\frac{r^2}{2r} = \frac{r}{2}$ , and therefore that (because the capacitance of the origin is 2)


$$p_{\text{esc}}^{(r)} = \frac{1}{r}.$$

The limit as  $r$  goes to infinity of this quantity is 0; therefore, this walk is recurrent.


**Theorem 4** *The two-dimensional lattice graph  $\mathbb{Z}^2$  is recurrent.*

**Proof.** Take our graph, turn it into an electrical network with origin =  $(0, 0)$ , and perform the following really clever trick: for every  $r$ , let  $V_r$  be the collection of all of the vertices that are distance  $r$  from the origin under the taxicab metric (i.e. shortest length of a path.) Take our graph and **short** all of  $V_r$ 's vertices into one huge clump, for each  $r$ : i.e. take the collection of all of the vertices at distance  $r$ , and just stick them all together! We know that this reduces the overall resistance, because of Rayleigh's principle; therefore, we know that if this graph is recurrent,  $\mathbb{Z}^2$  must be as well.

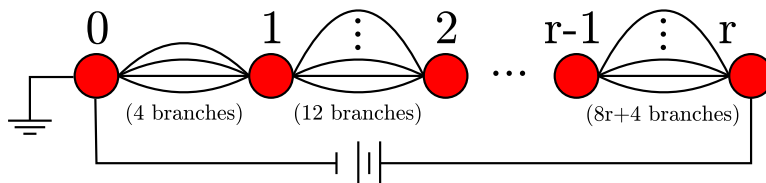What does this process do to the restricted graph  $(\mathbb{Z}^2)^{(r)}$ ? Well, it produces the following picture:



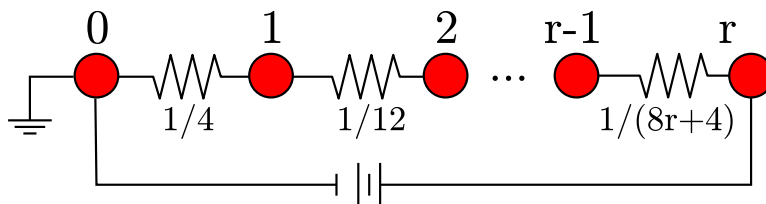What is the resistance here? Well: there are  $8n+4$  resistors between node  $n$  and node  $n+1$ ; therefore, this graph is equivalent to the path on  $\{0, \dots, r\}$  where the resistance between  $n$  and  $n+1$  is  $\frac{1}{8n+4}$ :



Therefore, we can see that the limit of the resistance of these  $r$ -restricted graphs is the sum

$$\sum_{i=1}^r \frac{1}{8i + 4},$$

which goes to infinity; therefore, the current on these graphs and thus the  $p_{\text{esc}}^{(r)}$ 's go to 0. So this graph is also recurrent.

**Lemma 5** *Suppose  $C$  is a circuit with two vertices  $x, y$  that are not connected by a resistor and are at the same potential: i.e.  $v(x) = v(y)$ . Then shorting together  $x$  and  $y$  does not change the voltages or currents in the circuit.*


**Proof.** HW!

**Theorem 6** *The three-dimensional lattice graph  $\mathbb{Z}^3$  is transient.*


**Proof.** For  $\mathbb{Z}^2$ , the trick we used was to “short” a bunch of vertices together, and show that the resulting graph (which was simpler, even though its resistances were “lower”) was recurrent. Here, in  $\mathbb{Z}^3$ , we’re going to “cut” a number of resistors, and show that the resulting (simpler, higher-resistance) graph is transitive! (The normal proof of this theorem is much more difficult without these observations; it’s only with this “shorting” and “cutting” that we can pull this off with such relative ease<sup>1</sup>.)

Specifically: lattices are **hard** to calculate resistances on. Let’s try something simpler: a tree!

Well, we should be careful what tree we mean. For example, consider the infinite binary tree graph  $T_2$ , where each edge is a resistor of resistance 2. Notice that (by symmetry) all of the nodes at any fixed distance  $k$  from the origin have the same potential: therefore, we can short them all together without changing anything in our graph. If we take this graph and cut it off at its first  $r$  nodes, we have the following picture:

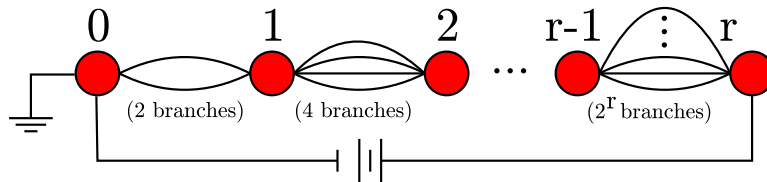

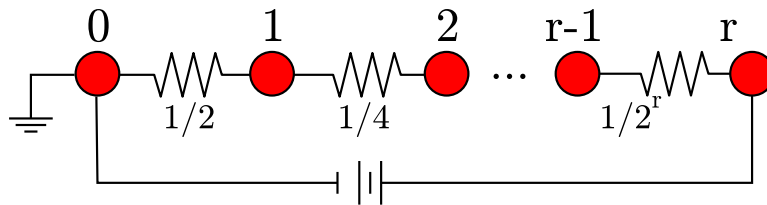We can therefore use our earlier observations on resistors in parallel to turn this into the following circuit:




<sup>1</sup>Insert your own “short-cut” pun here.

This has resistance  $\sum 1/2^n = 1$ . Winning!

Kind-of. See, the number of nodes in a binary tree grows like  $2^n$ , whereas the number of nodes distance  $n$  from the origin grows like  $n^2$ : so we're never going to be able to find a binary tree in  $\mathbb{Z}^3$ ! Whatever will we do?


We will be **clever**. Specifically, let's stay with the tree structure. Binary was overkill: the sum  $\sum 1/2^n$  converges far faster than we need! We just need a tree who splits often enough that we'll get \*some\* sort of convergent thing at the end of the day.

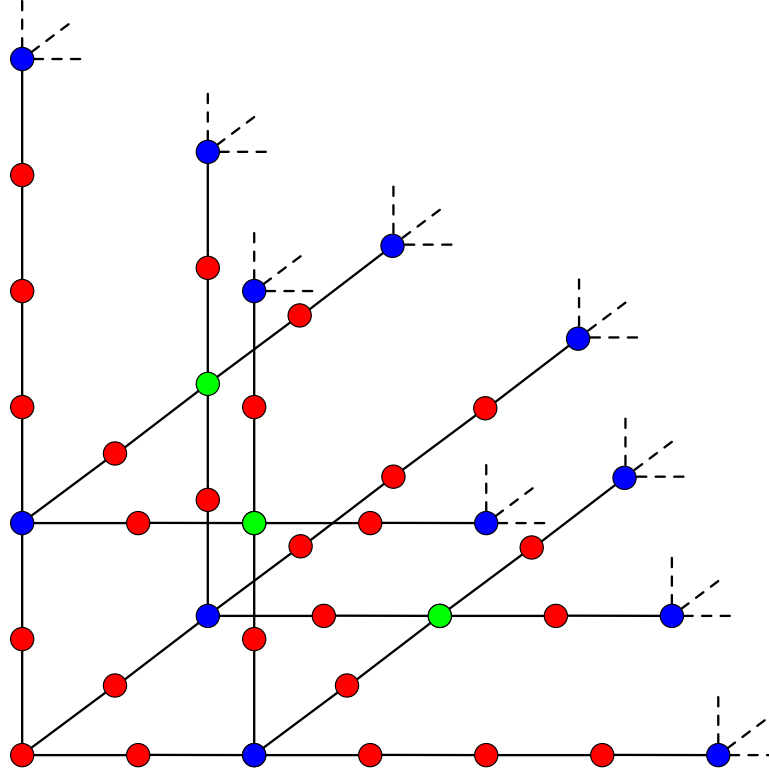To do this, consider the following kind of "tree:"



As currently drawn: not a tree. However, if you pretend that each of the green nodes are "doubled", by creating two vertices at each of those locations and passing only one branch through each node, it's a tree! Furthermore, because these nodes are at the same distances from the origin, we know that they have the same voltage passing through them by symmetry! This tree branches at distances  $\sum_{n=1}^r 2^n$  for every  $r \geq 1$  (i.e. at the blue nodes,) and creates three branches (one in the  $x, y$  and  $z$  directions) at each such distance. By construction, these branches never intersect at these "branching" blue nodes: therefore, this tree is realizable in  $\mathbb{Z}^3$  as depicted above.

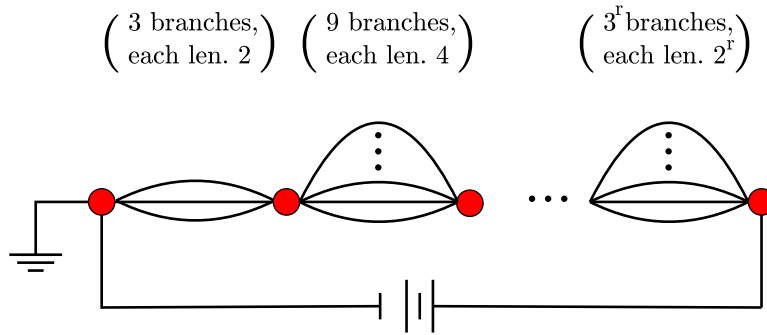By identifying nodes of distance  $\sum_{n=1}^r 2^n$  for every  $n$  from the origin, the graph on this tree restricted to the distances  $\sum_{n=1}^r 2^n$  is equivalent to a circuit of the form



By applying our known results about resistors in series and parallel, we can see that the total resistance between any two nodes  $n - 1, n$  in the above circuit is

$$\frac{2^n}{3^n};$$

therefore, our tree at stage  $R$  has total resistance

$$\sum_{n=1}^r \frac{2^n}{3^n} = \frac{1 - (2/3)^{r+1}}{1 - (2/3)} - 1.$$

As  $r$  goes to infinity, this goes to 2; therefore, the current  $i_b = v(b)/R_{\text{eff}} = 1/2$  at infinity is positive, and consequently the value  $p_{\text{esc}} = i_b/C_b = \frac{1/2}{3} = 1/6$  is positive and nonzero. Therefore, by our earlier discussion, there is a nonzero chance of escape! In other words, our random walker may never return to the origin

This allows us to finally answer the question we've designed this class around:

**Corollary 7** *If you've lost a piffle somewhere on an integer lattice, it will come back home if and only if it cannot fly.*